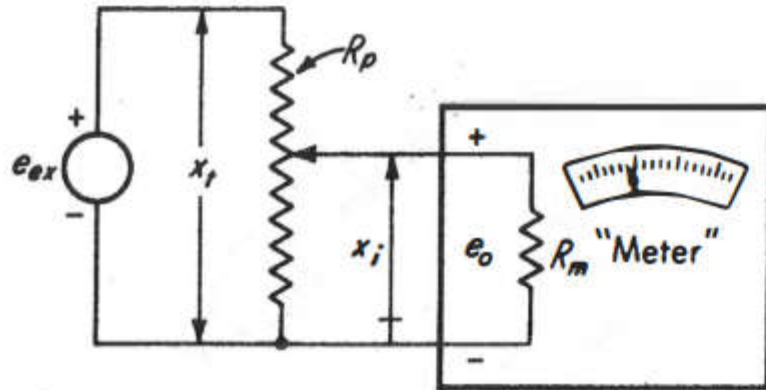


# **Theory of some important Transducers**

## Analysis of Potentiometer Circuit



$$\frac{e_o}{e_{ex}} = \frac{1}{1/(x_i/x_t) + R_p/R_m)(1 - x_i/x_t)}$$

For an ideal meter,  $R_m$  will be infinite then one may have  $R_p/R_m$  will be almost zero

Then one may write

$$\frac{e_o}{e_{ex}} = \frac{x_i}{x_t}$$

