
# Theory of some important Transducers


# Measurement of Displacement
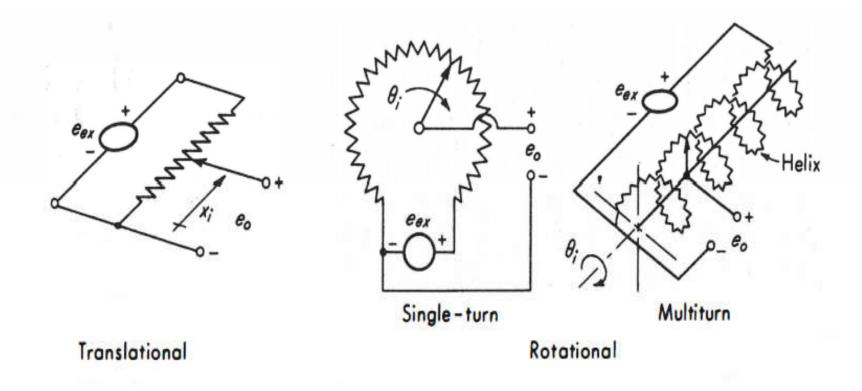
# **Measurement of Displacement by Potentiometer**




#### **Potentiometer Construction**



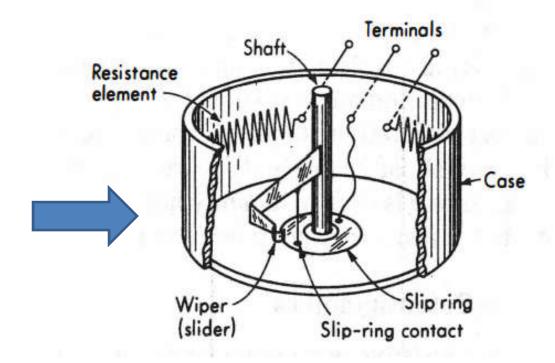
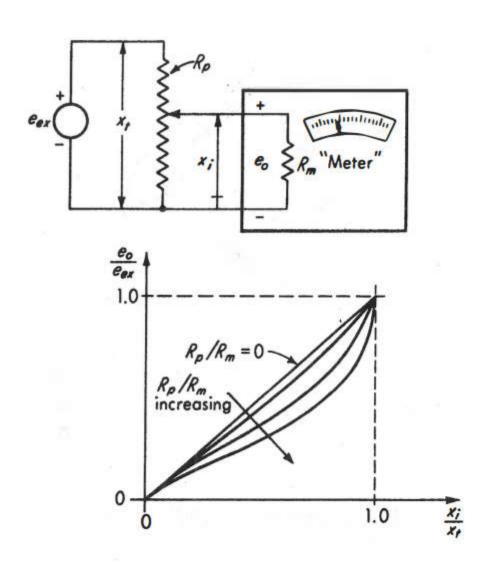
#### **Analysis of Potentiometer Circuit**




$$\frac{e_o}{e_{ex}} = \frac{1}{1/(x_i/x_t) + R_p/R_m)(1 - x_i/x_t)}$$

For an ideal meter, Rm will be infinite then one may have Rp/Rm will be almost zero

Then one may write

$$\frac{e_o}{e_{ex}} = \frac{x_i}{x_t}$$


#### **Application of Potentiometer**

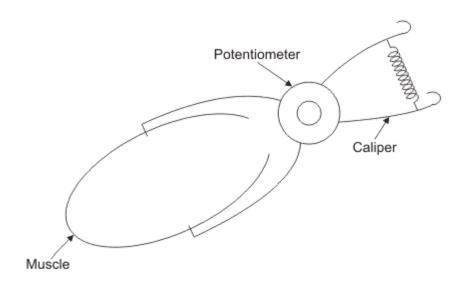

To detect the changes in the chest (Thoracic) circumference, rotary potentiometer is attached to a chest band on a person.

In this setup, the transducer acts as a pivot to the caliper arms.

# **Strain Gauge**

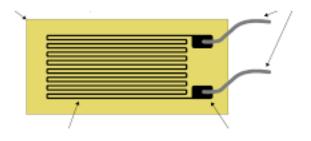

#### Measurement of Strain by Resistance Strain Gauge

Consider a conductor of uniform cross-sectional area A and length L, made of a material with resistivity  $\rho$ . The resistance R of such a conductor is given by

$$R = \frac{\rho L}{A}$$

Partially differentiating the above equation w.r.t  $\rho$ , L and A , we have

$$dR = \frac{L d\rho}{A} + \frac{\rho dL}{A} - \frac{\rho L dA}{A^2}$$

Dividing dR with R one may have

$$\frac{dR}{R} = \frac{d\rho}{\rho} + \frac{dL}{L} - \frac{dA}{A}$$

As  $A = \pi D^2$ 

Thus one may write the above equation as

$$\frac{dR}{R} = \frac{d\rho}{\rho} + \frac{dL}{L} - 2\frac{dD}{D}$$

Since the change is very small, one can modify the equation as


$$\frac{\triangle R}{R} = \frac{\triangle \rho}{\rho} + \frac{\triangle L}{L} - 2 \frac{\triangle D}{D}$$

Gauge factor G can be defined as


$$G = \frac{\frac{\triangle R}{R}}{\frac{\triangle L}{L}} = (1 + 2v) \quad \text{Poisson's Ratio } v = -\frac{\frac{\triangle D}{D}}{\frac{\triangle L}{L}}$$

Here Piezoresistive effect is neglected

#### **Types of Strain Gauge**

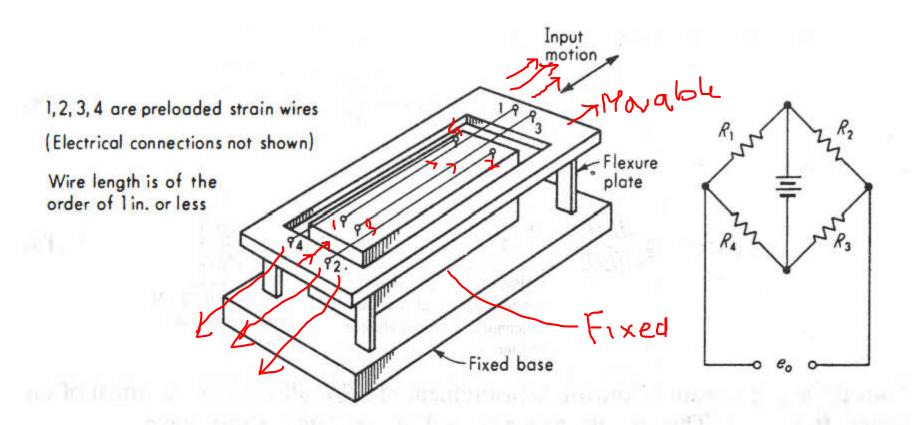

Unbonded strain gage

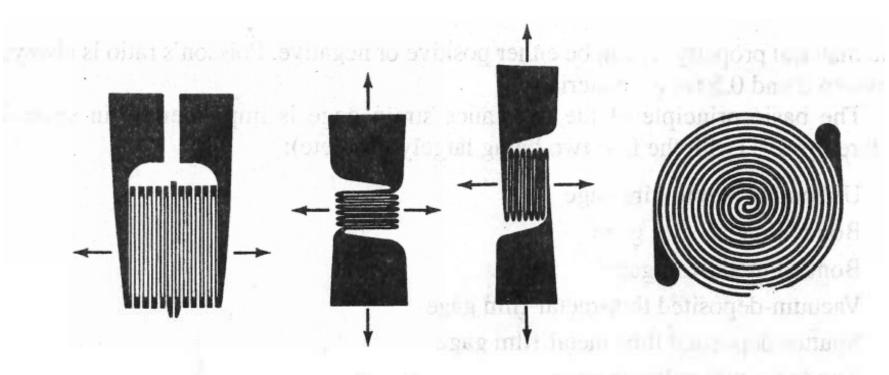


and semico in claims bestflist

Foil strain gages.

# **Circuit with one active Strain Gauge**


Gauge in tension 
$$(R_0 + \Delta R)$$
  $V_{\text{EX}}$   $V_{\text{O}}$   $V_{\text{O}}$ 

#### **Temperature Compensation**

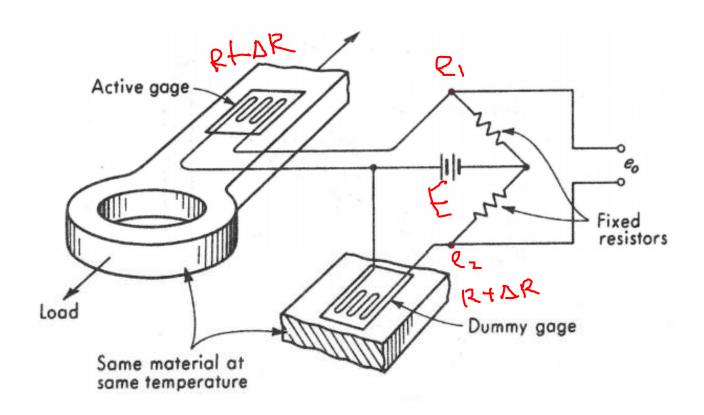


Strain-gage temperature compensation.
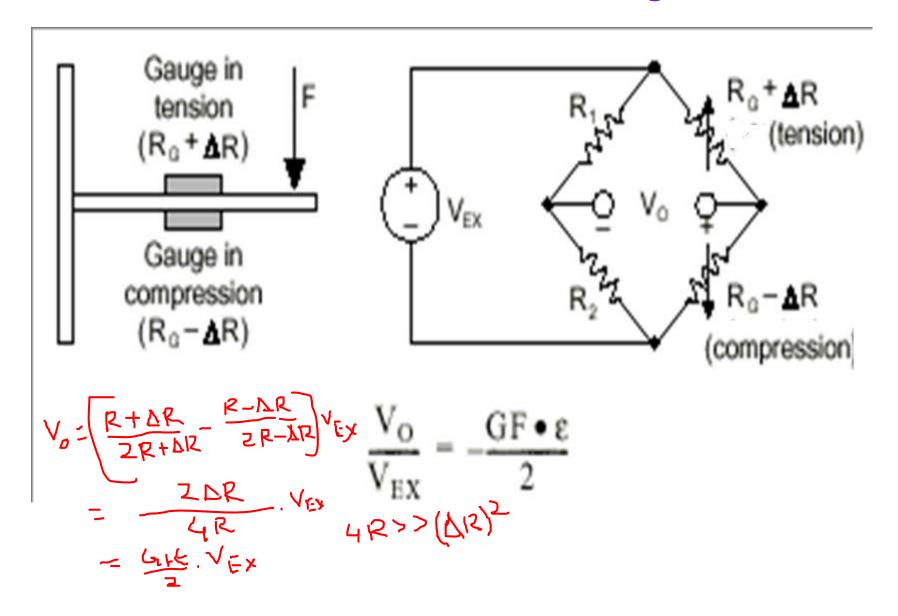
# **Circuit with two active Strain Gauges**



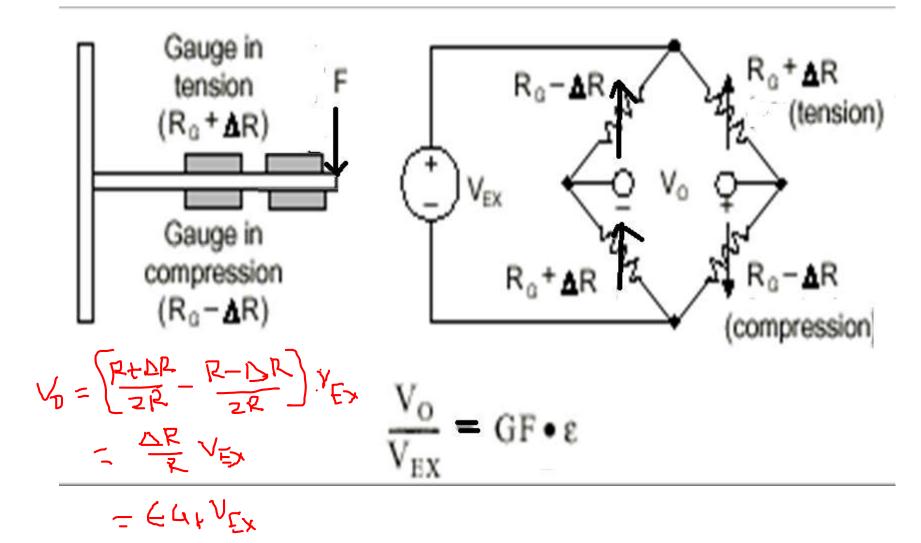
# **Circuit with four active Strain Gauges**



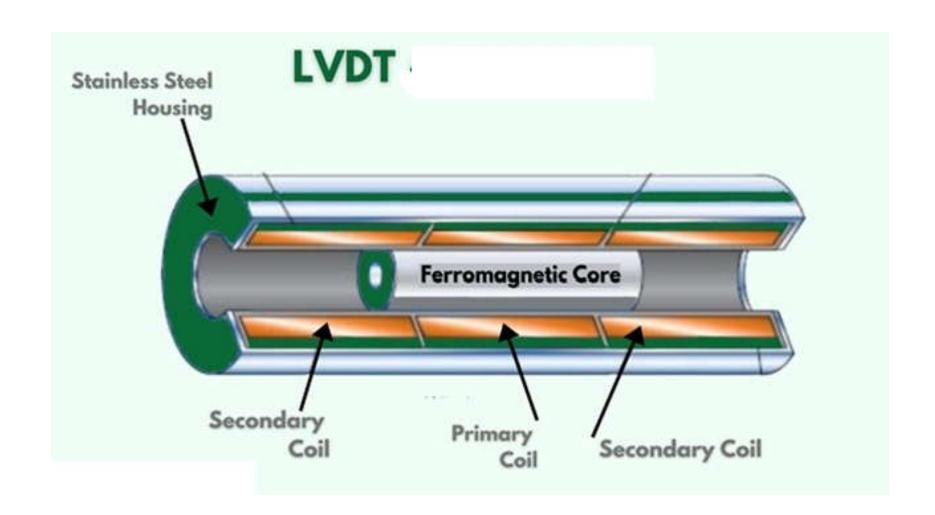
#### **Application of Strain Gauge**


- Strain gauge measures the blood pressure inside the heart or blood vessels to diagnose cardiovascular abnormalities.
- The strain gauge is attached to the tip of the catheter
- The catheter is injected into the heart through veins
- On the front side of strain gauge diaphragm is mounted which undergoes deflection due to the applied force due to blood
- Therefore, when blood pressure inside the heart varies, it deflects the diaphragm that in turn changes the strain gauge resistance.



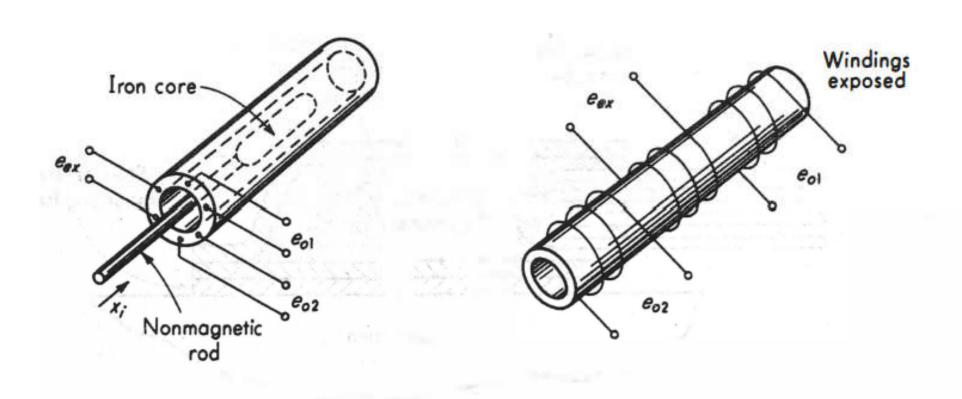
# **Measurement of displacement by LVDT**




**LVDT Construction** 

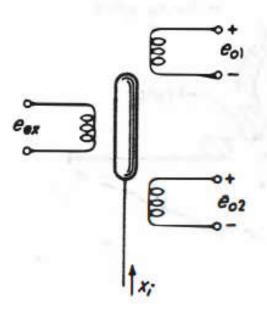


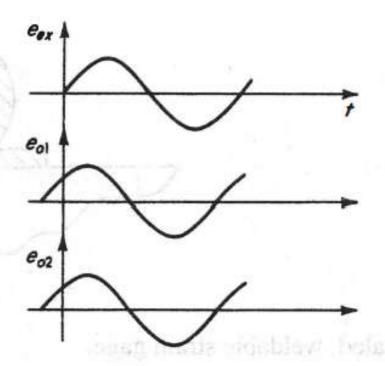


Core in null position



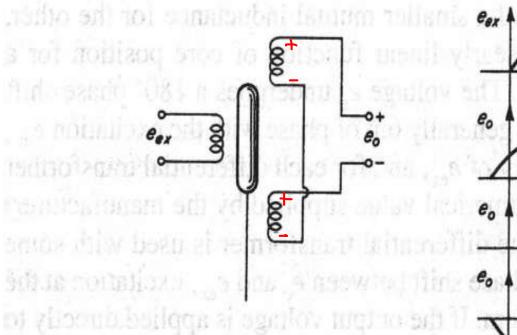


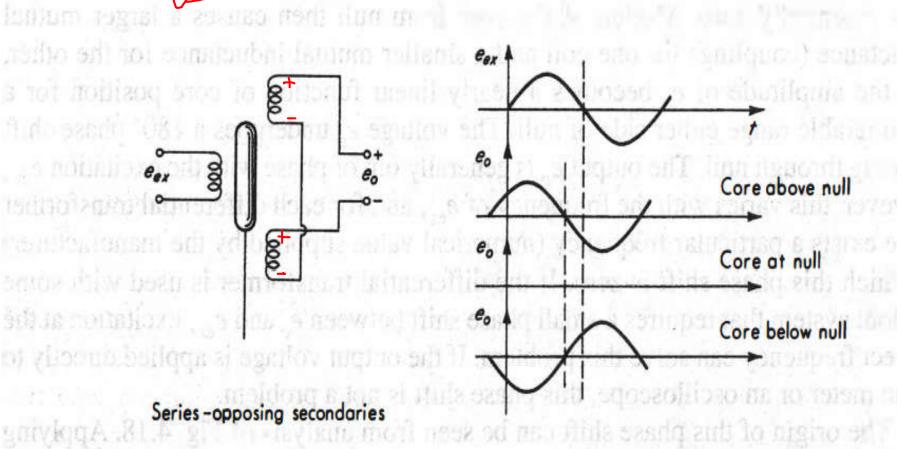


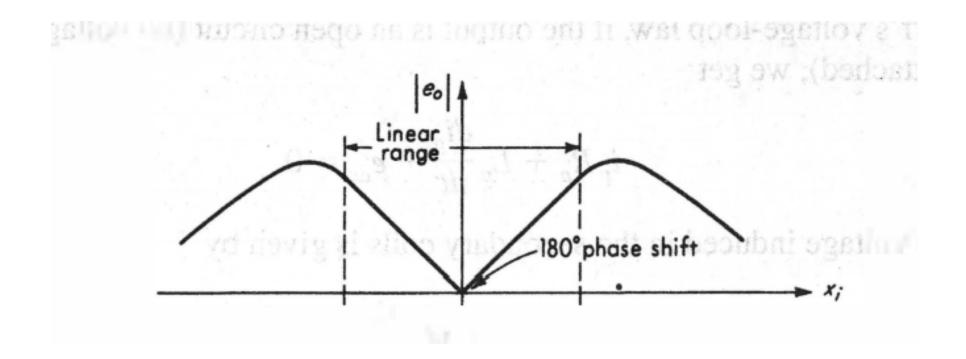

**Output Vs Input of LVDT** 

# **Circuit Analysis of LVDT**

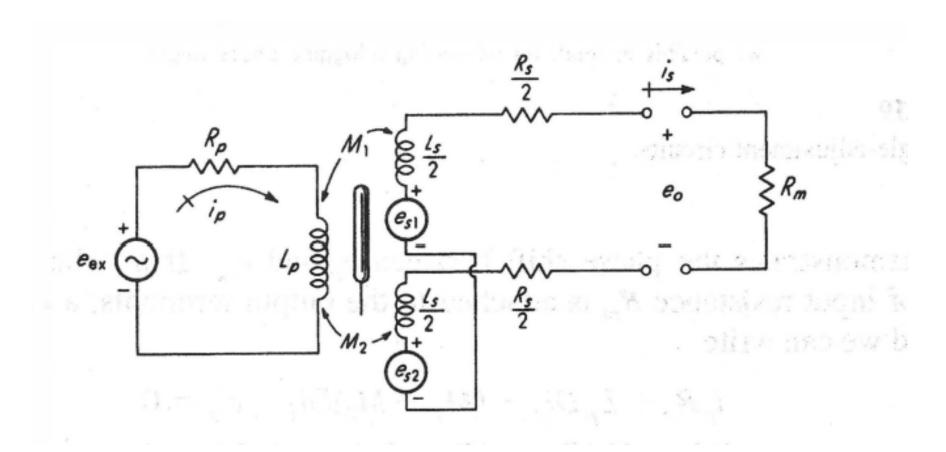

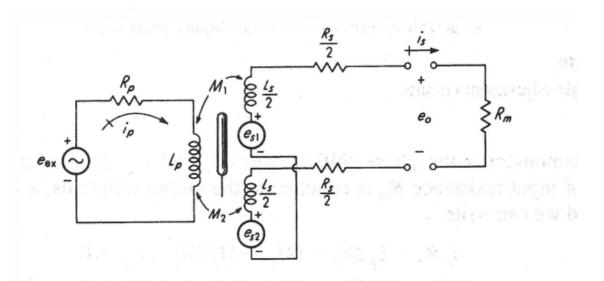


Applying Kirchhoff's voltage-loop law, if the output is an open circuit (no voltage-measuring device attached), we get

$$i_p R_p + L_p \frac{di_p}{dt} - e_{ex} = 0 (1)$$

Now the voltage induced in the secondary coils is given by

$$e_{s1} = M_1 \frac{di_p}{dt}$$

$$e_{s2} = M_2 \frac{di_p}{dt}$$
(2)

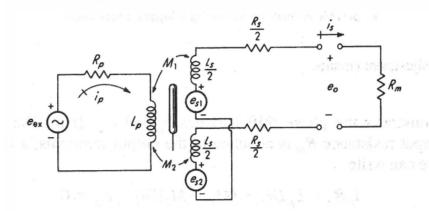

 $M_1$  and  $M_2$  are the respective mutual inductances. The net secondary voltage e, is then given by

$$e_s = e_{s1} - e_{s2} = (M_1 - M_2) \frac{di_p}{dt}$$
 (3)

The net mutual inductance  $M_1 - M_2$  is the quantity that varies linearly with core motion. We have for a fixed core position

$$e_o = e_s = (M_1 - M_2) \frac{D}{L_p D + R_p} e_{ex}$$
 (4)

and thus

$$e_{o} = e_{s} = (M_{1} - M_{2}) \frac{D}{L_{p}D + R_{p}} e_{ex}$$

$$\frac{e_{o}}{e_{ex}}(D) = \frac{[(M_{1} - M_{2})/R_{p}]D}{\tau_{p}D + 1} \qquad \tau_{p} \triangleq \frac{L_{p}}{R_{p}}$$
(5)

In terms of frequency response,

$$\frac{e_o}{e_{ex}}(i\omega) = \frac{\omega(M_1 - M_2)/R_p}{\sqrt{(\omega \tau_p)^2 + 1}} \angle \phi \qquad \phi = 90^\circ - \tan^{-1} \omega \tau_p \qquad (6)$$

If a voltage-measuring

device of input resistance  $R_m$  is attached to the output terminals, a current  $i_s$  will flow, and we can write


$$i_p R_p + L_p D i_p - (M_1 - M_2) D i_s - e_{ex} = 0 (7)$$

$$(M_1 - M_2)Di_p + (R_s + R_m)i_s + L_sDi_s = 0$$
 (8)


which lead to

$$\frac{e_o}{e_{ex}}(D) = \frac{R_m(\dot{M_2} - M_1)D}{[(M_1 - M_2)^2 + L_p L_s]D^2 + [L_p(R_s + R_m) + L_s R_p]D + (R_s + R_m)R_p}$$
(9)

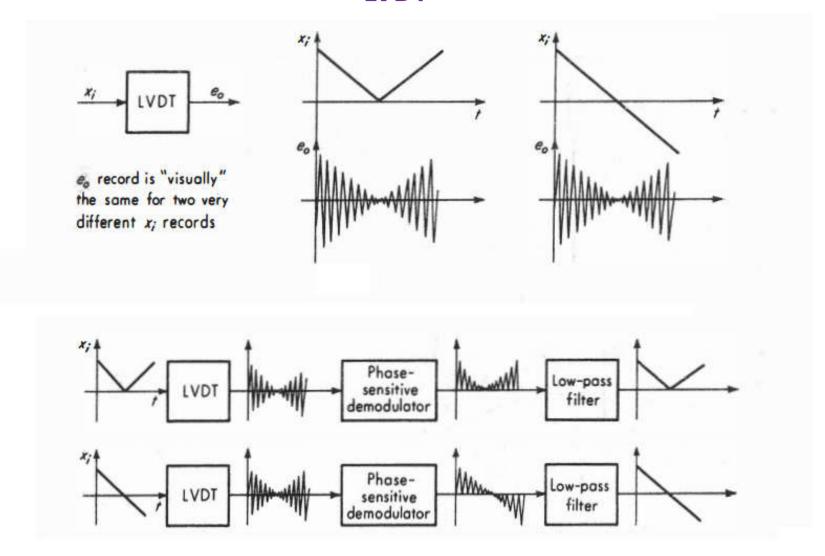
# Requirement of Phase Sensitive Demodulation in LVDT



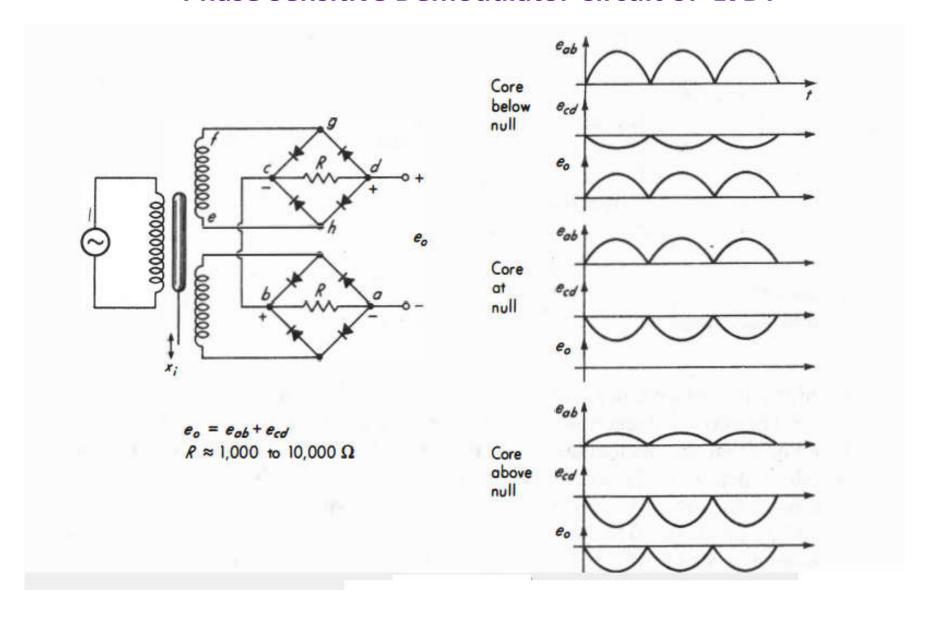
#### **Phase Sensitive Demodulator Circuit of LVDT**


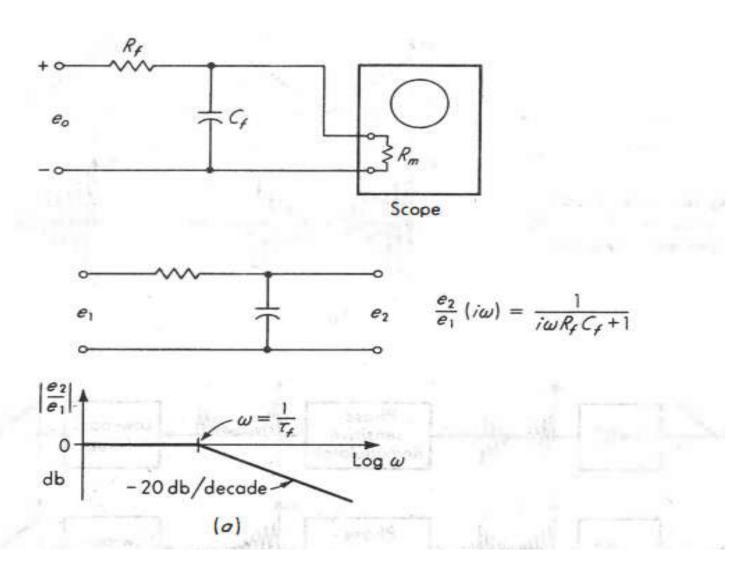
# **Low pass Filtering of Demodulator output**



1<sup>st</sup> Order LPF response

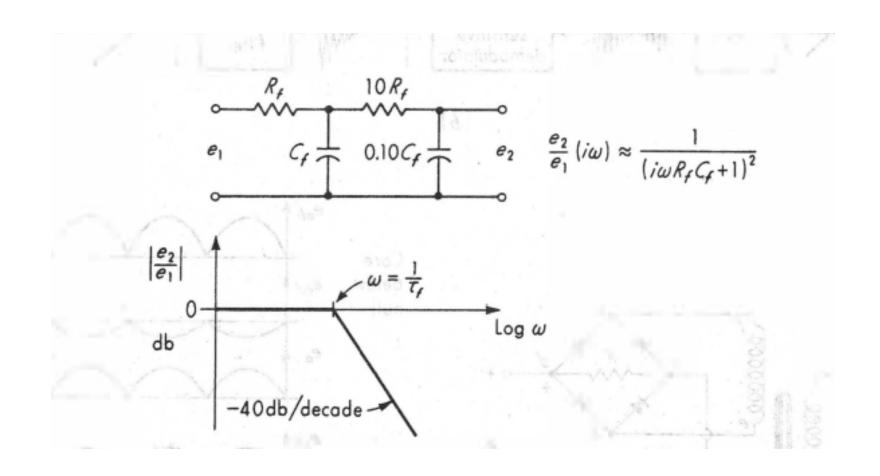

2<sup>nd</sup> Order LPF response

#### **Application of LVDT**

☐ Transduction of respiration through changes in chest volume

☐ Measuring dimensional change of internal organ